



AAKASH ELECTRONICS
EST. 1994 • SP ROAD, BENGALURU

CATALOGUE 18

ICs & audio modules.

Timer, regulator, op-amp, logic and interface ICs, plus a deep stock of TDA, LA, STK, AN, UM and KA series audio power ICs for repair and amplifier work. Thirteen plates, every part stocked at the counter.

13

SUBSECTIONS

13


PLATES

75

ITEMS LISTED

Timer ICs


4 ITEMS

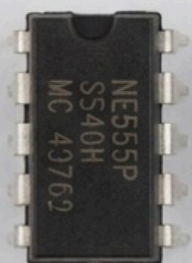

1) NE555 Timer



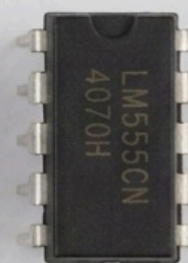2) Wider DIP-14 — caption "NE556 Dual Timer"



3) LM555 Timer



4) ICM7555 CMOS Timer

ITEMS • PART NUMBER IN BRACKETS

01 NE555 Timer IC [NE555]


02 NE556 Dual Timer IC [NE556]

03 LM555 Timer IC [LM555]


04 ICM7555 CMOS Timer [ICM7555]

Voltage Regulator ICs


6 ITEMS

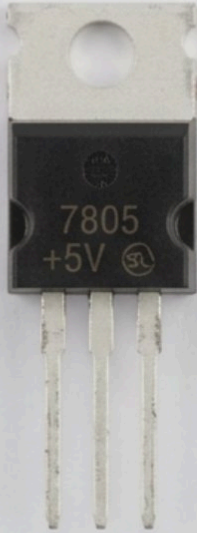

1) 7805 +5V Regulator

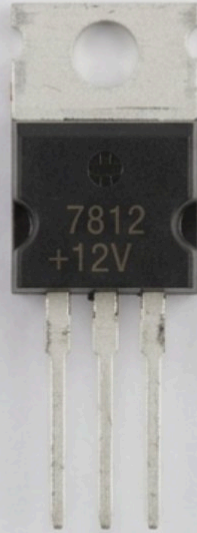

2) 7812 +12V Regulator

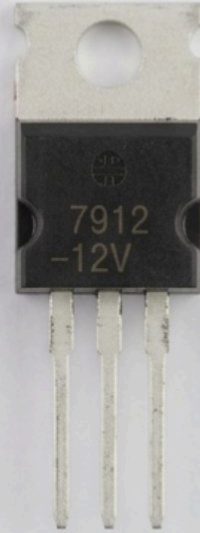

3) 7912 -12V Regulator



4) LM317 Adjustable

5) tiny SMD SOT-223 —
SMD SOT-223 — caption “AMS1117-3.3 LDO”6) tiny SMD SOT-223 —
caption “AMS1117-5.0 LDO”

ITEMS · PART NUMBER IN BRACKETS

- 01 7805 +5V Linear Voltage Regulator [L7805CV]
- 02 7812 +12V Linear Voltage Regulator [L7812CV]
- 03 7912 -12V Linear Voltage Regulator [L7912CV]
- 04 LM317 Adjustable Voltage Regulator [LM317]
- 05 AMS1117-3.3 Low-Dropout Regulator (SMD) [AMS1117-3.3]
- 06 AMS1117-5.0 Low-Dropout Regulator (SMD) [AMS1117-5.0]

Op-Amps & Comparators

9 ITEMS



1) LM741 Op-Amp



2) LM358 Dual Op-Amp



3) LM324 Quad Op-Amp



4) LM393 Comparator




5) LM311 Comparator



6) TL071 Op-Amp




7) TL072 Dual Op-Amp

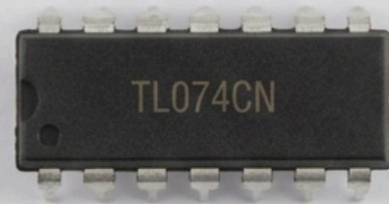

8) TL074 Quad Op-Amp



7) TL072 Dual Op-Amp

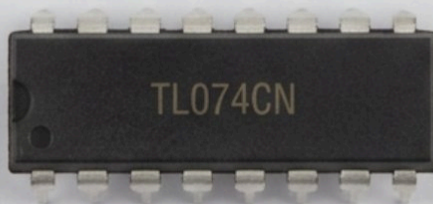

8) TL074 Quad Op-Amp



9) LM386 Audio Amp

ITEMS · PART NUMBER IN BRACKETS

01 LM741 Single Op-Amp [LM741]

02 LM358 Dual Op-Amp [LM358]

03 LM324 Quad Op-Amp [LM324]

04 LM393 Dual Comparator [LM393]

05 LM311 Single Comparator [LM311]

06 TL071 Low-Noise Op-Amp [TL071]


07 TL072 Dual Low-Noise Op-Amp [TL072]

08 TL074 Quad Low-Noise Op-Amp [TL074]


09 LM386 Audio Amplifier IC [LM386]

Motor Driver & Darlington Array ICs

5 ITEMS

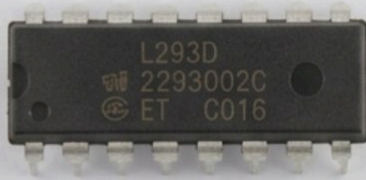

1) L293D H-Bridge

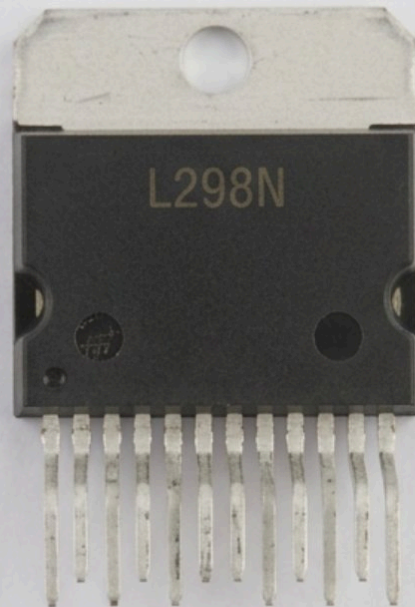

2) wider Multiwatt15 flat-tab — caption "L298N Dual H-Bridge"




3) ULN2003A Darlington



4) ULN2003A Darlington



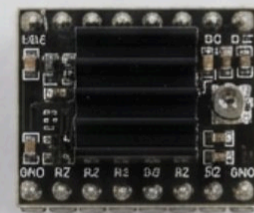4) wider DIP-18 — caption "ULN2803A Darlington"



5) A4988 Stepper Driver

ITEMS • PART NUMBER IN BRACKETS

- 01 L293D H-Bridge Motor Driver [L293D]
- 02 L298N Dual H-Bridge Driver [L298N]
- 03 ULN2003A Darlington Array [ULN2003A]
- 04 ULN2803A Darlington Array [ULN2803A]
- 05 A4988 Stepper Motor Driver (IC) [A4988-IC]

Logic, Shift Register & Interface ICs (74HC)

11 ITEMS



1) 74HC595 Shift Register



2) 74HC165 Shift Register



3) 74HC138 Decoder



4) 74HC04 Hex Inverter



5) 74HC14 Schmitt Inverter



6) 74HC00 NAND Gate



7) 74HC08 AND Gate



8) 74HC32 OR Gate



9) 74HC86 XOR Gate



10) MAX232 RS-232



11) MAX485 RS-485 — (DIP-8)

ITEMS • PART NUMBER IN BRACKETS

01 74HC595 8-Bit Shift Register [74HC595]

02 74HC165 8-Bit Parallel-In Shift Register [74HC165]

03 74HC138 3-to-8 Line Decoder [74HC138]

04 74HC04 Hex Inverter [74HC04]

05 74HC14 Hex Schmitt-Trigger Inverter [74HC14]

06 74HC00 Quad 2-Input NAND [74HC00]

07 74HC08 Quad 2-Input AND [74HC08]

08 74HC32 Quad 2-Input OR [74HC32]


09 74HC86 Quad 2-Input XOR [74HC86]

10 MAX232 RS-232 Level Shifter [MAX232]

11 MAX485 RS-485 Transceiver [MAX485]

USB, Interface & Power Management ICs


6 ITEMS

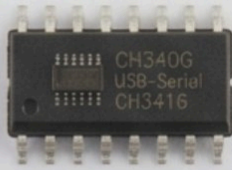

1) CH340G USB-Serial



2) CP2102 USB-UART

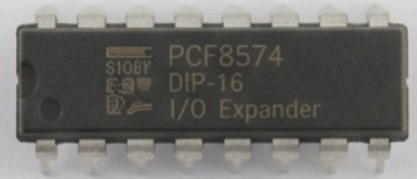


3) PCF8574 I/O Expander



4) MCP23017 I/O Expander




5) TP4056 Li-ion Charger

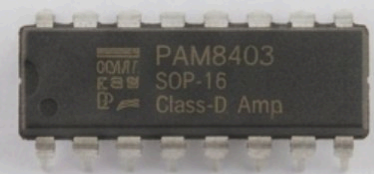

6) PAM8403 Class-D Amp



4) MCP23017 I/O Expander

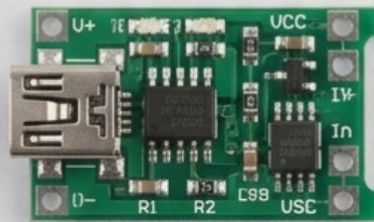

5) TP4056 Li-ion Charger



6) PAM8403 Class-D Amp



4) MCP23017 I/O Expander




6) PAM8403 Class-D Amp

ITEMS · PART NUMBER IN BRACKETS

- 01 CH340G USB-to-Serial Bridge IC [CH340G]
- 02 CP2102 USB-to-UART Bridge IC [CP2102]
- 03 PCF8574 8-Bit I/O Expander (I2C) [PCF8574]
- 04 MCP23017 16-Bit I/O Expander (I2C/SPI) [MCP23017]
- 05 TP4056 Li-ion Battery Charger IC (Module) [TP4056]
- 06 PAM8403 Class-D Audio Amplifier IC [PAM8403]

TDA Series — Audio Power Amplifier ICs

9 ITEMS

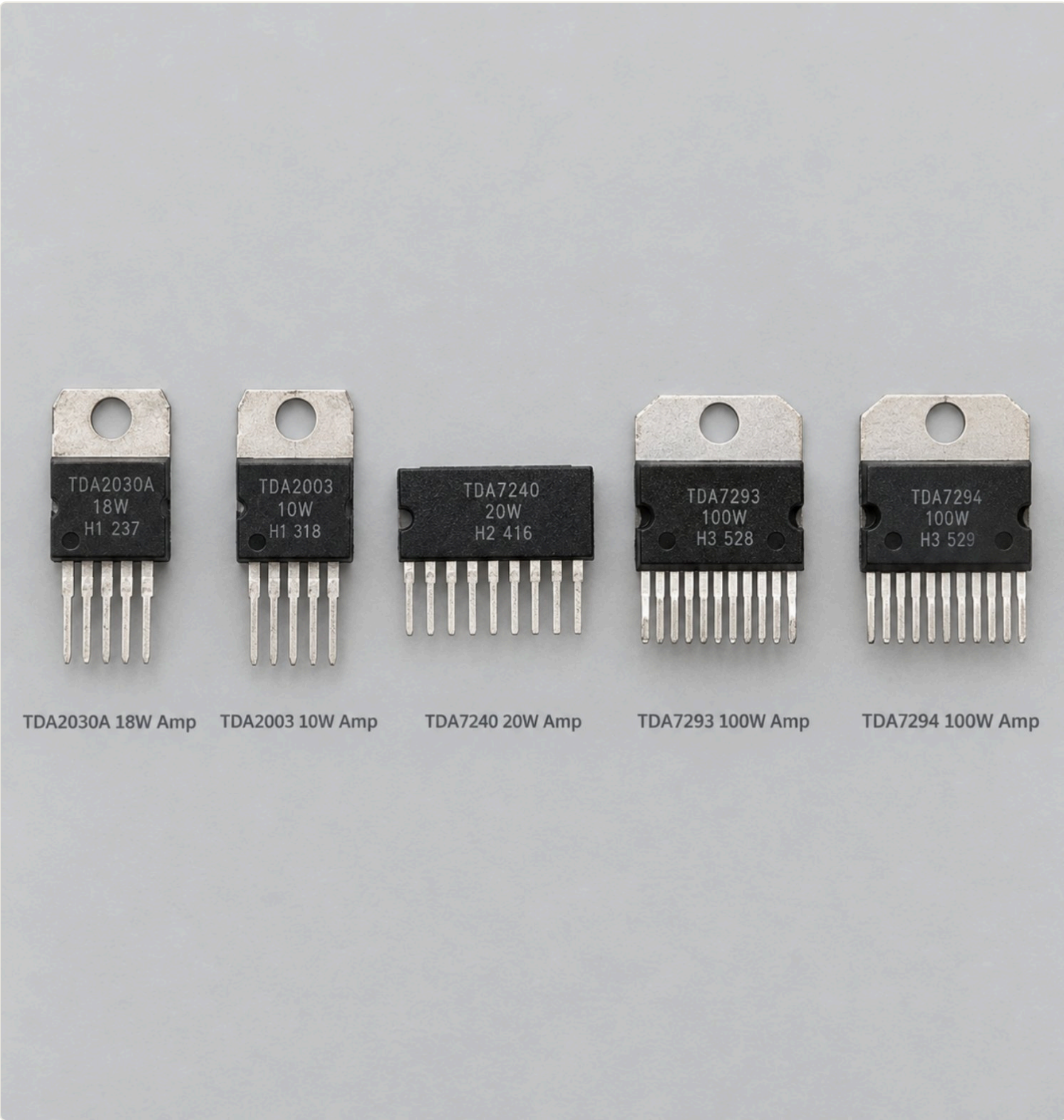

ITEMS · PART NUMBER IN BRACKETS

- 01

TDA2030A Audio Amplifier [TDA2030A]
- 02

TDA2003 Audio Amplifier [TDA2003]
- 03

TDA7240 Audio Power Amplifier [TDA7240]
- 04

TDA7293 Audio Power Amplifier [TDA7293]
- 05

TDA7294 Audio Power Amplifier [TDA7294]
- 06

TDA7388 Quad Bridge Amplifier [TDA7388]
- 07

TDA8340 / TDA8341 TV Deflection IC [TDA8340]
- 08

TDA1554 Dual-Bridge Car Amp [TDA1554]
- 09

TDA1557Q Dual-Bridge Amp [TDA1557Q]

LA Series — Sanyo Audio ICs

4 ITEMS



TDA7388 Quad Bridge



TDA8340 TV Deflection



TDA1554 Dual-Bridge




TDA1557Q Dual-Bridge

ITEMS • PART NUMBER IN BRACKETS


- 01 LA4440 Dual/Bridge Audio Amplifier [LA4440]
- 02 LA4550 Dual Power Amplifier [LA4550]
- 03 LA5522 Voltage Regulator IC [LA5522]
- 04 LA7837 Vertical Deflection IC [LA7837]

STK Series — Sanyo Hybrid Power ICs

4 ITEMS

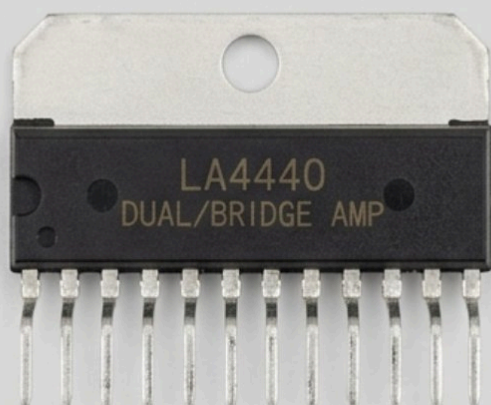


LA4440 Dual/Bridge Amp

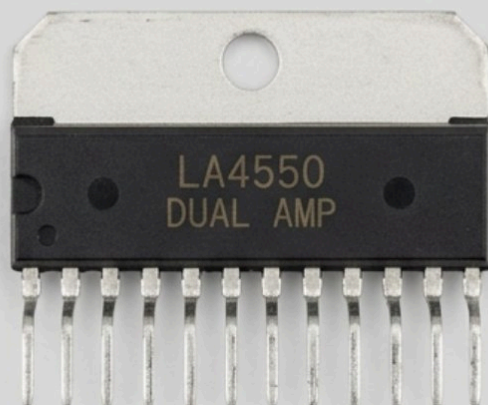

LA4550 Dual Amp



LA5522 Voltage Regulator

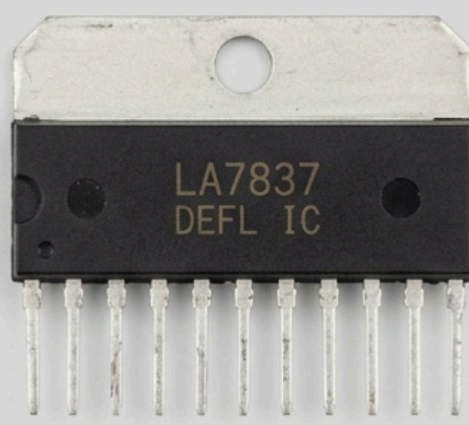

LA7837 Deflection IC

ITEMS · PART NUMBER IN BRACKETS

- 01 STK4191 Stereo Power Amplifier [STK4191]
- 02 STK4525 Stereo Power Amplifier [STK4525]
- 03 STK7594 Switching Regulator IC [STK7594]
- 04 STK18B (STK18 Series) Power IC [STK18B]

AN Series — Panasonic Audio ICs

4 ITEMS



STK4191 Stereo Amp



STK4525 Stereo Amp



STK7594 Switching Reg



STK18B Power IC

ITEMS · PART NUMBER IN BRACKETS


- 01 AN7521 Audio Amplifier [AN7521]
- 02 AN5532 Dual Low-Noise Op-Amp [AN5532]
- 03 AN6612 FM IF / Detector IC [AN6612]
- 04 AN7168 Power Amplifier [AN7168]

UM / UPC Series — NEC / Rohm ICs

4 ITEMS



AN7521 Audio Amp

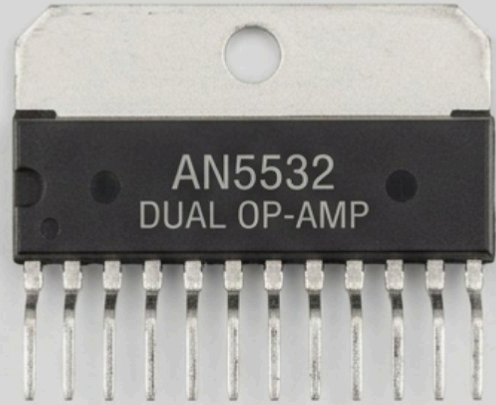

AN5532 Dual Op-Amp



AN6612 FM IF Detector



AN7168 Power Amp

ITEMS · PART NUMBER IN BRACKETS

- 01 UM3750 CMOS Encoder/Decoder [UM3750]
- 02 UM3761 Melody IC (multi-tone) [UM3761]
- 03 UM66T Melody Generator IC [UM66T]
- 04 UPC1003 / UPC1032 Audio IC [UPC1003]

KA / HA Series — Samsung / Hitachi ICs


3 ITEMS



UM3750 Encoder/Decoder



UM3761 Melody IC

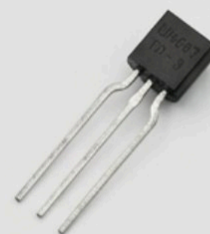

UM66T Melody Generator



UPC1003 Audio IC



KA2263 Tone Control



KA2284 Level Meter



HA1196 Stereo Decoder

ITEMS • PART NUMBER IN BRACKETS


01 KA2263 Tone Control IC [KA2263]

02 KA2284 Level Meter IC [KA2284]

03 HA1196 Stereo Decoder IC [HA1196]

74LS / 74HC Logic Series

6 ITEMS

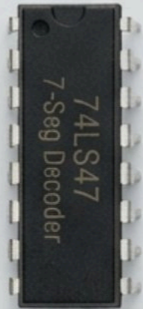

74LS47
7-Seg Decoder



74LS74
D Flip-Flop



74LS93
Binary
Counter



74LS173
D-Register



CD4017
Decade
Counter



CD4013
D Flip-Flop

ITEMS • PART NUMBER IN BRACKETS

- 01 74LS47 BCD-to-7-Segment Decoder [74LS47]
- 02 74LS74 Dual D Flip-Flop [74LS74]
- 03 74LS93 4-Bit Binary Counter [74LS93]
- 04 74LS173 4-Bit D-Type Register [74LS173]
- 05 CD4017 CMOS Decade Counter [CD4017]
- 06 CD4013 Dual D Flip-Flop (CMOS) [CD4013]



ORDER OR ENQUIRE

Send your list, we will quote it.

This catalogue covers our IC and audio module range. Datasheets are shared over WhatsApp on request. Share your BOM over phone, email or WhatsApp for availability and pricing.

ADDRESS

#84/4, 1st Floor, N.G.M Plaza,
S.P Road, Bengaluru 560002

OPENING HOURS

Monday to Saturday, 10:00 to 20:00
Sunday closed

PHONE & WHATSAPP

+91 99800 22755

EMAIL & WEB

aakashelectronics.blr@gmail.com
aakashelectro.in

Need a quotation on a bulk order?

Send your BOM or list on WhatsApp or email and we will respond with availability and pricing.

+91 99800 22755

aakashelectronics.blr@gmail.com